

Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

BTECH
(SEM IV) THEORY EXAMINATION 2021-22
ELECTRONICS ENGINEERING

Time: 3 Hours

Total Marks: 100

Note: Attempt all Sections. If you require any missing data, then choose suitably.

SECTION A

1. **Attempt all questions in brief.** **2x10 = 20**

Qno	Questions	CO
(a)	Si is preferred as compared to Ge in semiconductor devices. Justify this statement.	1
(b)	Describe the term PIV.	1
(c)	Enlist the application of LED.	2
(d)	Describe the tunneling phenomenon.	2
(e)	Derive the relationship between α and β for BJT.	3
(f)	Draw the transfer characteristics of JFET.	3
(g)	Describe the term CMRR and slew rate of an op-amp.	4
(h)	Enlist the characteristics of ideal op-amp.	4
(i)	Enlist the essential components of a CRT.	5
(j)	Explain the application of DSO.	5

SECTION B

2. **Attempt any three of the following:** **10x3 = 30**



Qno	Questions	CO
(a)	Explain the working of PN junction diode with no-bias condition, forward bias condition and reverse bias condition. Also draw the V-I characteristics of PN junction diode.	1
(b)	Illustrate the working of half wave rectifier using circuit diagram also determine its different parameter.	2
(c)	Mention the different biasing techniques used in BJT. Explain any two of them.	3
(d)	Draw the block diagram and equivalent circuit of an op-amp. Also explain op-amp as inverting and non-inverting amplifier.	4
(e)	Illustrate the working of digital multimeter with their block diagram.	5

SECTION C

3. **Attempt any one part of the following:** **10x1 = 10**

Qno	Questions	CO
(a)	Illustrate the diode resistance and diode capacitance.	1
(b)	Differentiate between Avalanche breakdown and Zener Breakdown mechanism.	1

4. **Attempt any one part of the following:** **10x1 = 10**

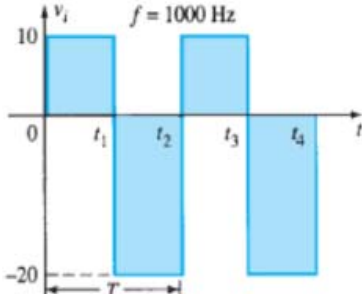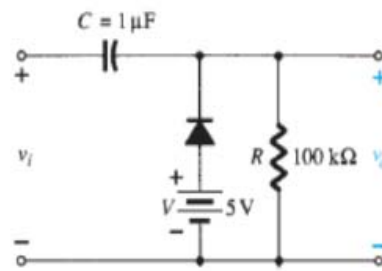Qno	Questions	CO
(a)	<p>Determine the output voltage and output waveform for a given input waveform. Assuming Silicon diodes.</p> <div style="display: flex; align-items: center;">   </div>	2



Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

BTECH
(SEM IV) THEORY EXAMINATION 2021-22
ELECTRONICS ENGINEERING

(b)	Explain the principle of operation and characteristics of an LED and Tunnel diode.	2
-----	--	---

5. Attempt any one part of the following: 10x1 = 10

Qno	Questions	CO
(a)	Draw the CE amplifier circuit and derive the expression for different characterizing parameters.	3
(b)	(i) Explain the construction and working of JFET. (ii) An enhancement type NMOS transistor with $V_t = 0.7$ V has its source terminal grounded and a 1.5 V applied to the gate. In what region does the device operate for a) $V_D = 0.5$ V b) $V_D = 0.9$ V c) $V_D = 3$ V.	3

6. Attempt any one part of the following: 10x1 = 10

Qno	Questions	CO
(a)	Draw the circuit diagram of an integrator and differentiator also find their output.	4
(b)	Illustrate the following op-amp parameters (i) input offset voltage (ii) output offset voltage (iii) input biased current (iv) input offset current (v) differential mode gain	4

7. Attempt any one part of the following: 10x1 = 10

Qno	Questions	CO
(a)	Describe measurement of voltage, current, frequency and phase using CRO.	5
(b)	Draw the block diagram of digital voltmeter. Also explain the ramp technique of digital multimeter.	5